

How to design a multiplier ?

TA: 蔡承佑

Contact: r10943014@ntu.edu.tw

How to compute $4*3$?


- **Easy ! Ans = $4+4+4 = 12$**
- **How about $4*5$?**
- **Ans = $4+4+4+4+4 = 20$**
- **The result of multiplication is the answer of successive addition.**

Software implementation

- **To compute $a*b$**
- **C++:**
 - **`ans = 0;`**
 - **`for(int i=0;i<b;++i)`
 - **`ans = ans + a;`****
- **Python**
 - **`ans = 0`**
 - **`for i in range(b):`
 - **`ans = ans + a`****

Hardware implementation ?

Does it work?

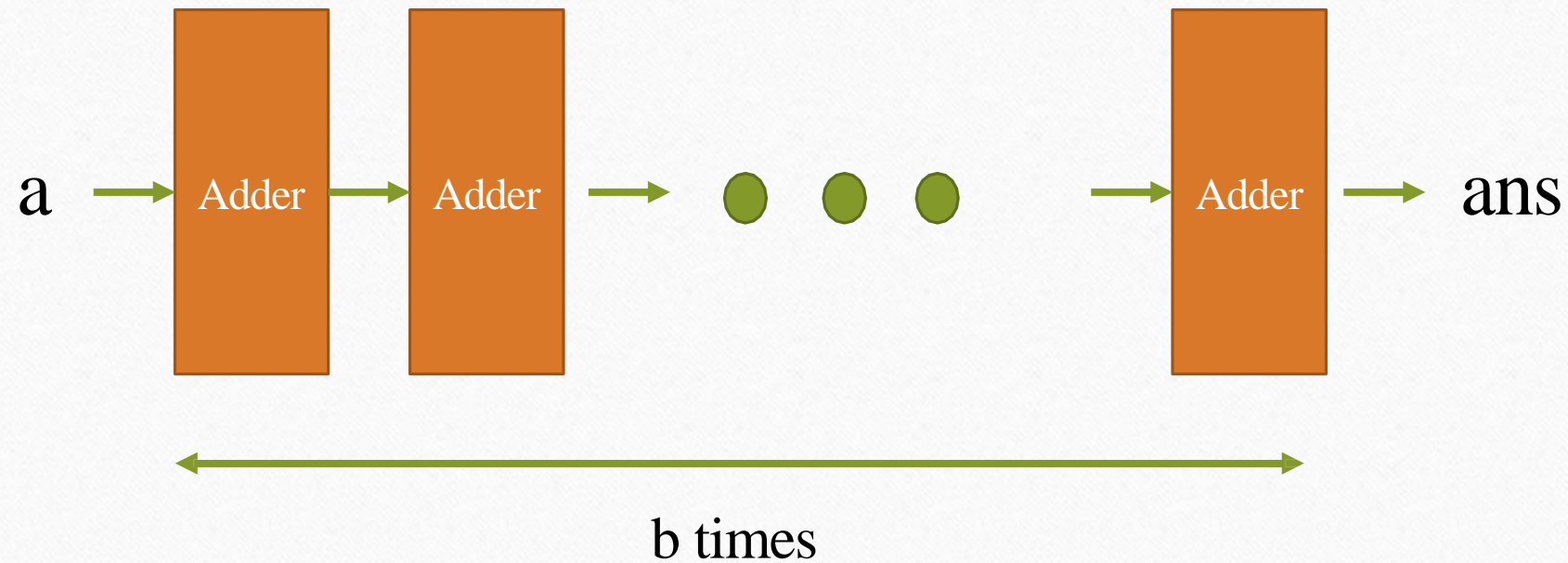


直式乘法


$$\begin{array}{r} 123 \\ x 264 \\ \hline 492 \\ 7380 \\ \hline 24600 \\ \hline 32472 \end{array}$$

$$\begin{array}{r} 1011 \\ x \underline{0110} \\ 0000 \\ 10110 \\ 101100 \\ \hline 0000000 \\ \hline 1000010 \end{array}$$


Multiplication Detail

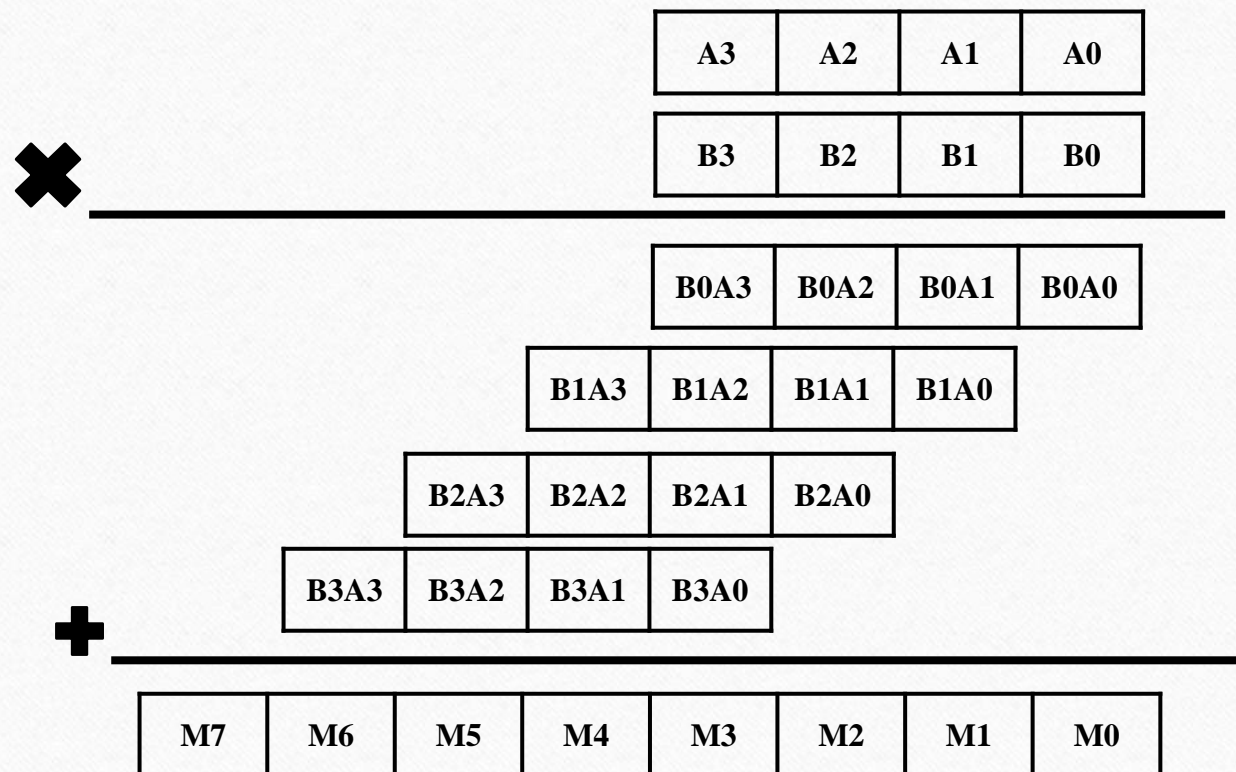


Step 1 compute trivial term

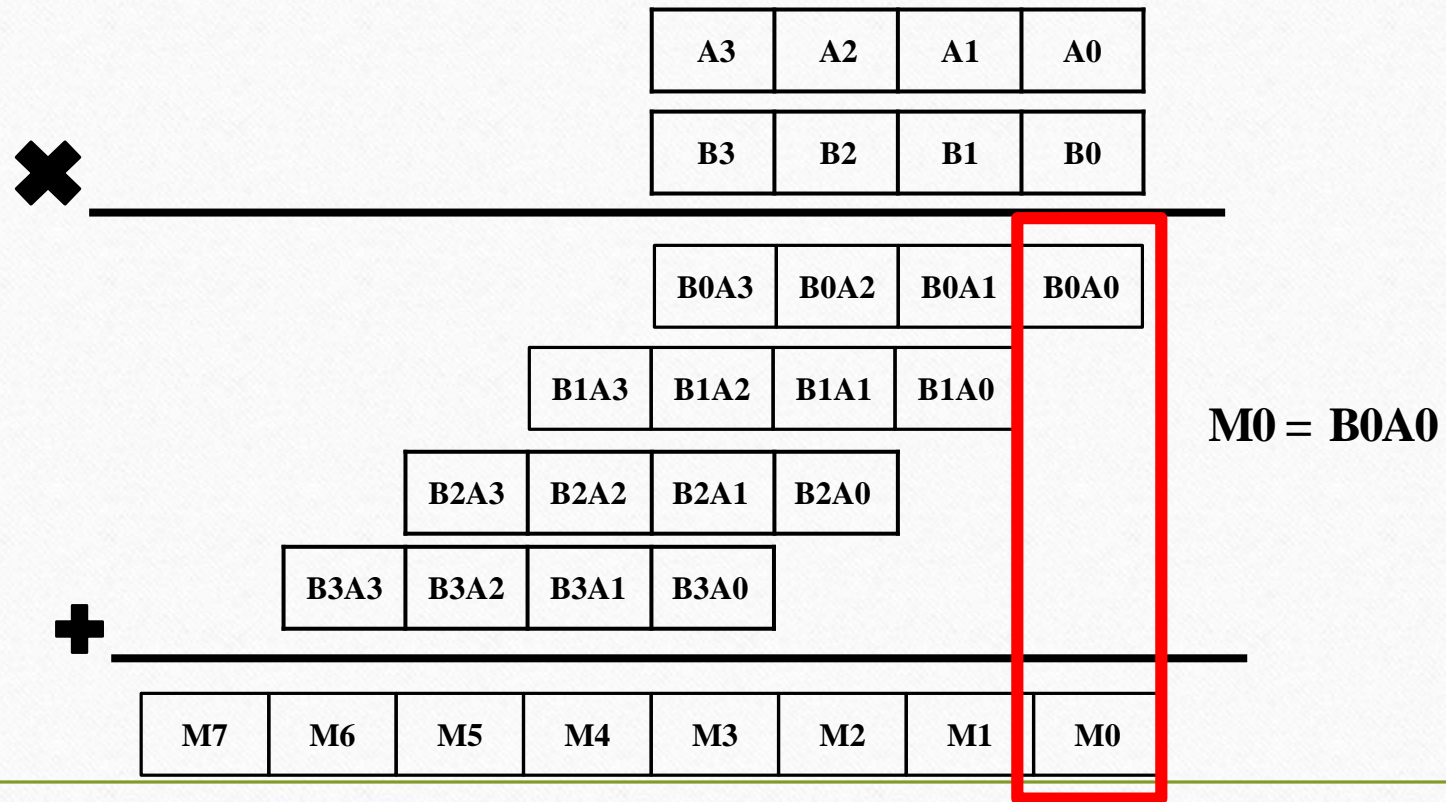


Step 2 compute partial sum

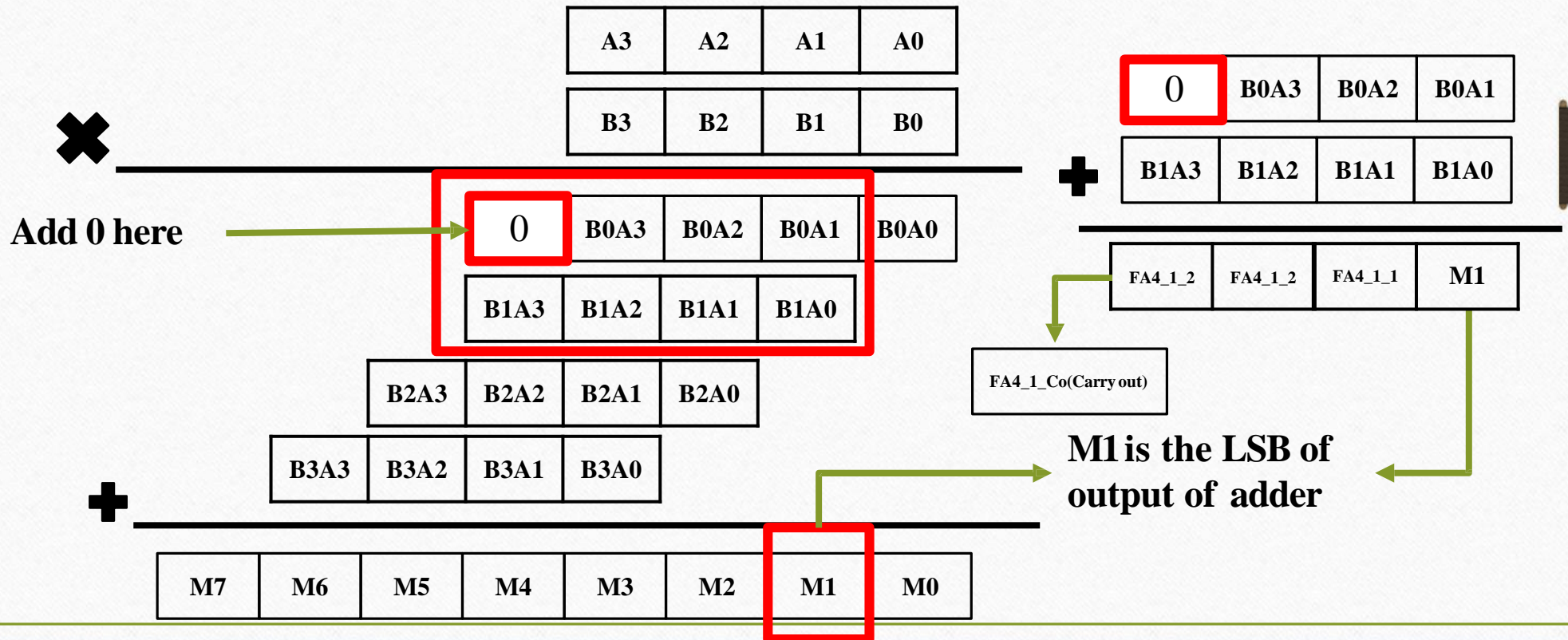


Step 2 compute partial sum(cont.)

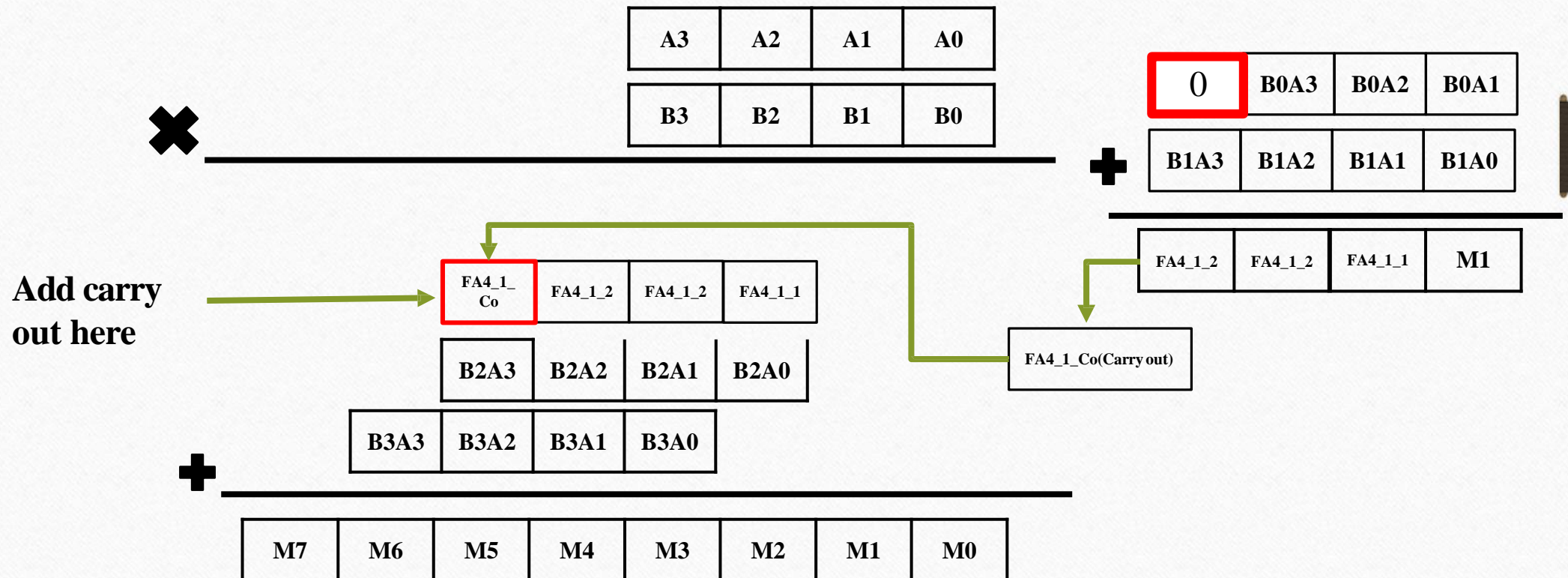

Step 2 compute partial sum(cont.)

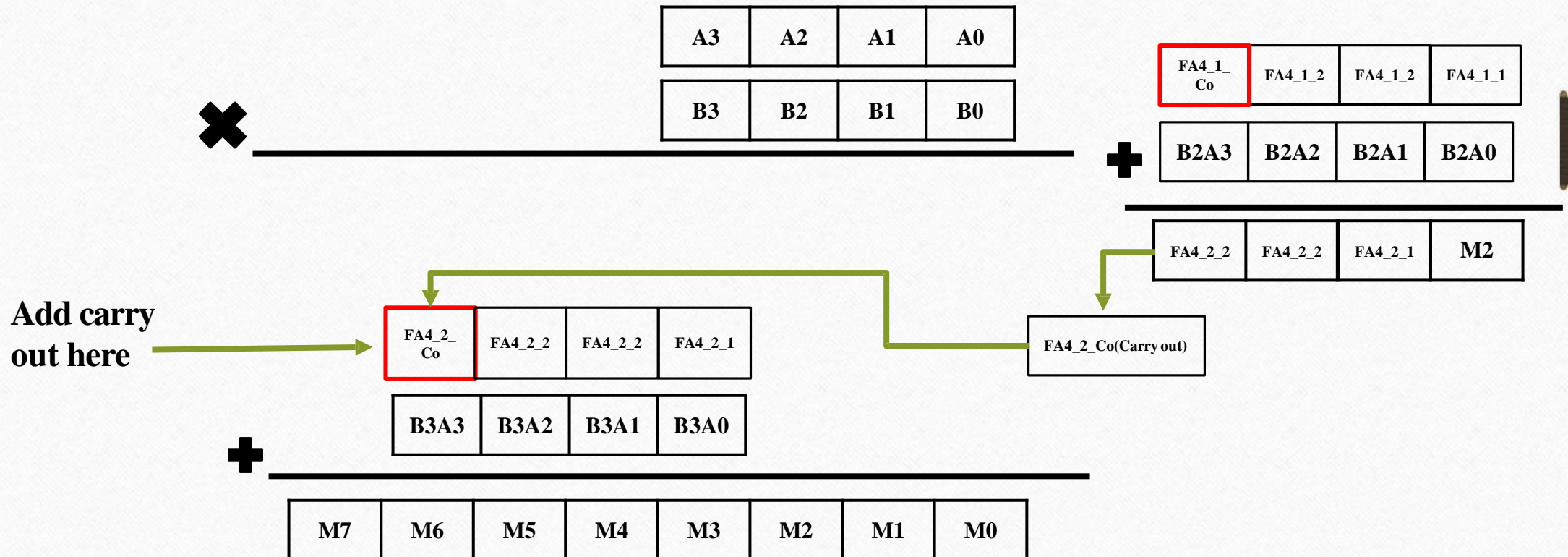

Step 2 compute partial sum(cont.)

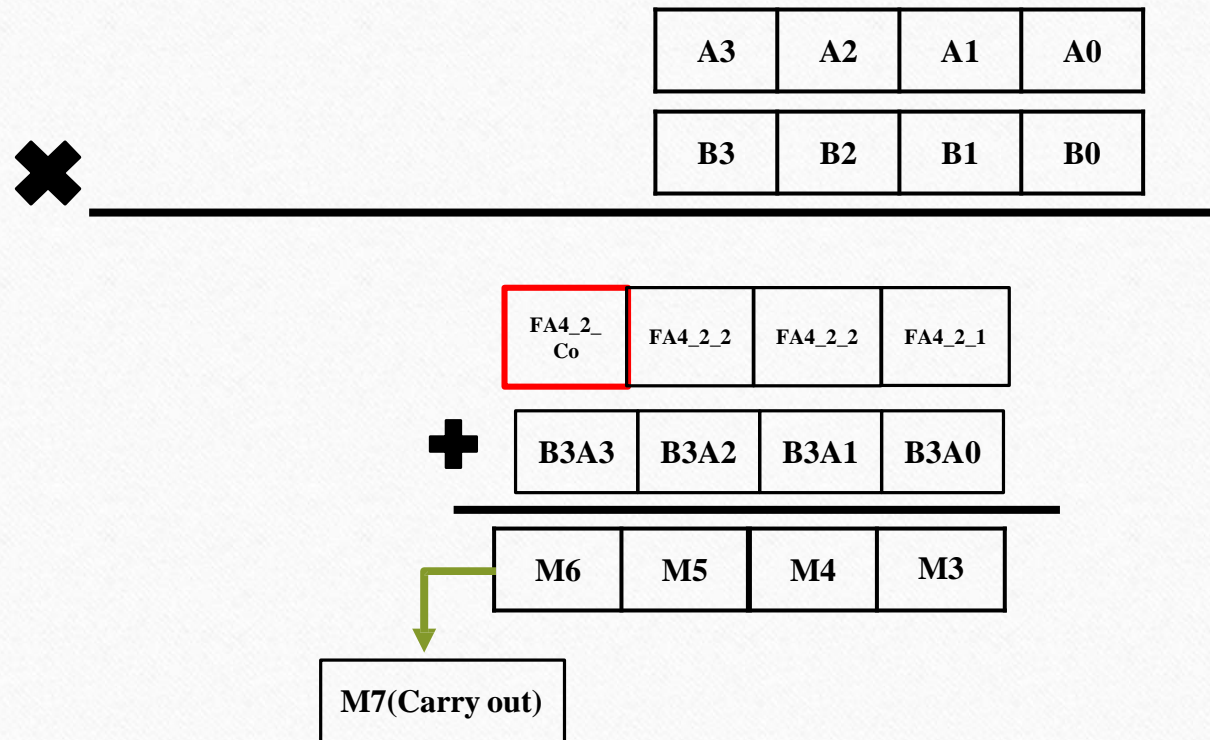

How to implement multiplier on Quartus II?

- Step 1: reuses your 4bits full adder, create a symbol of it. (FA4.bsf)

It's just an example, you can create it by your own way



Then, draw the circuit !!

Question?
