


Quartus II Lab2 — Sequential Circuits

NTU Switching Circuit and Logic Design 2023


B12902110 呂承諺

1 Lab2_1

1.1 SD: Sequence Detector

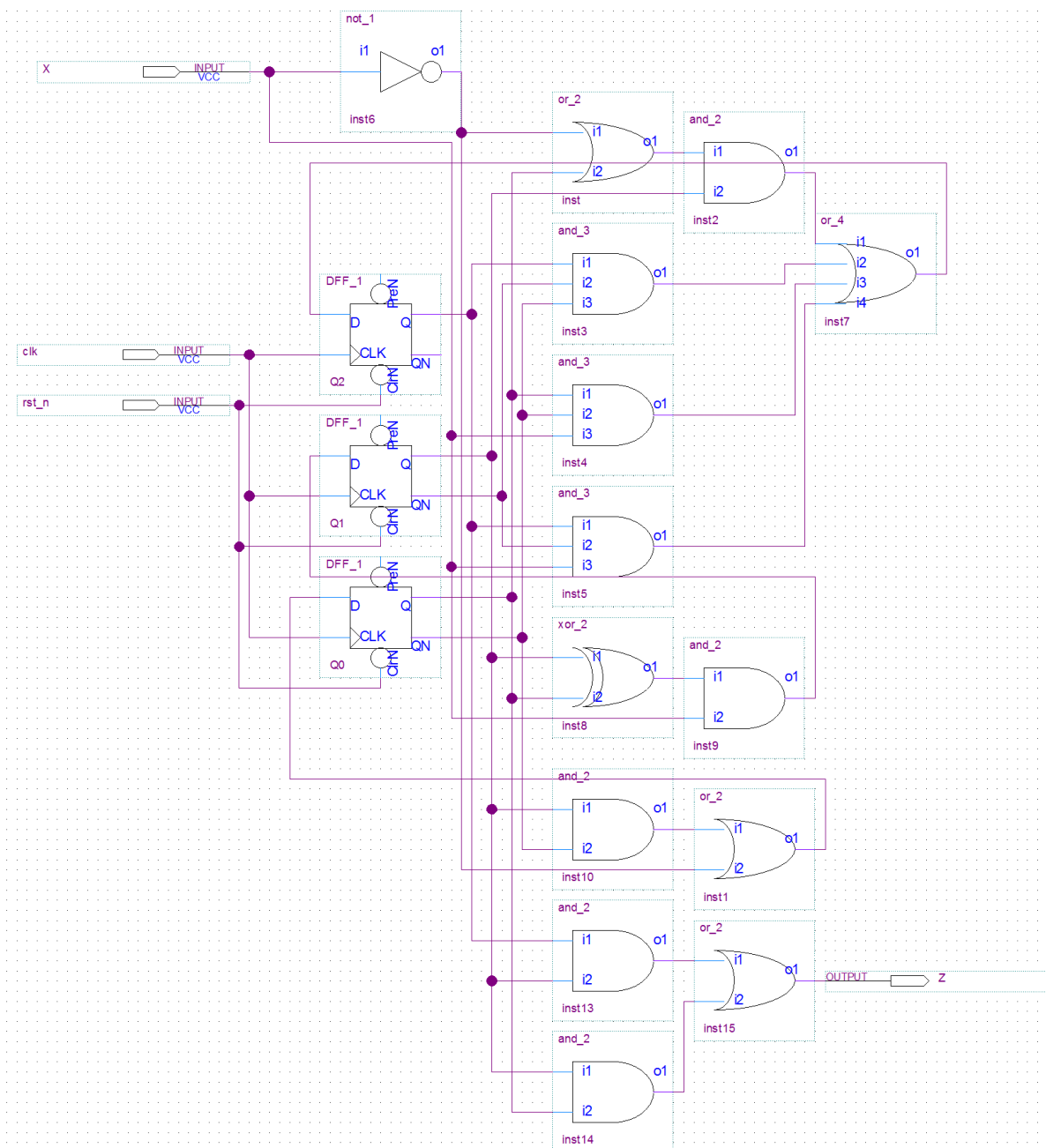


SD.bdf

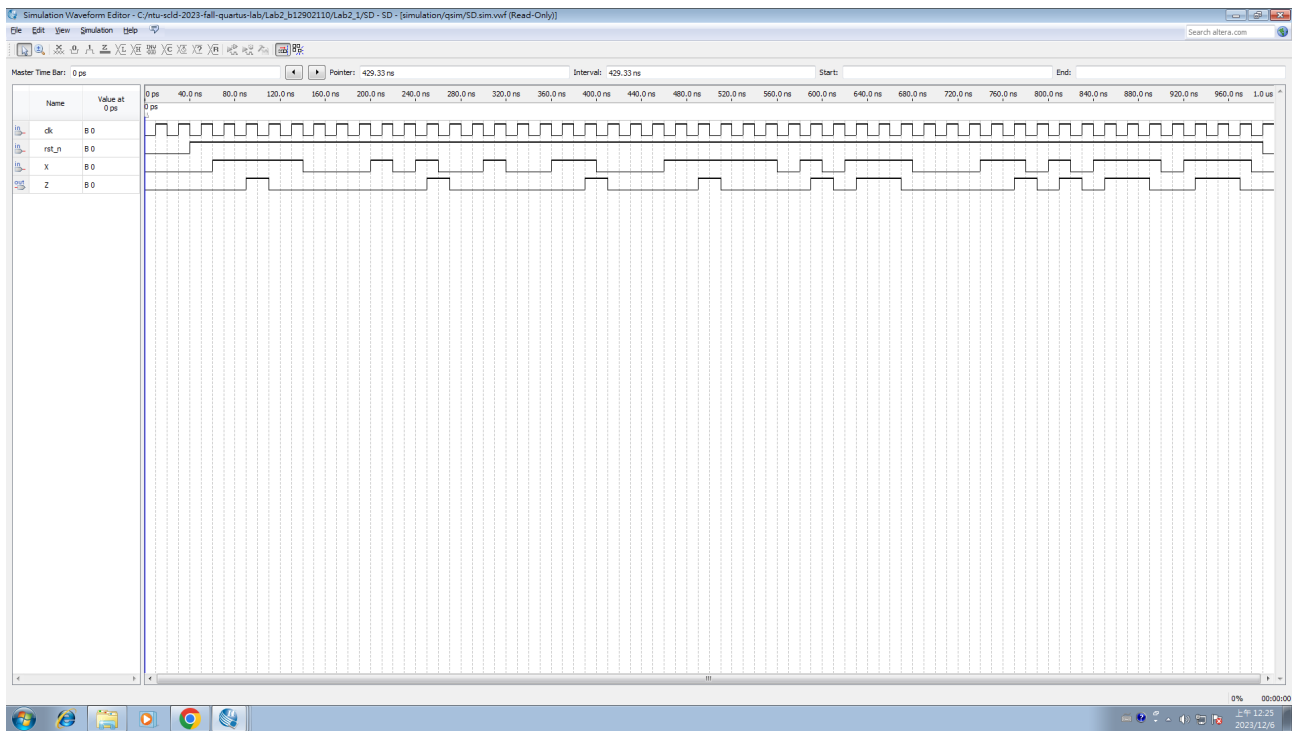


SD simulation result

2 Lab2_2


2.1 FA: 1-bit Full Adder

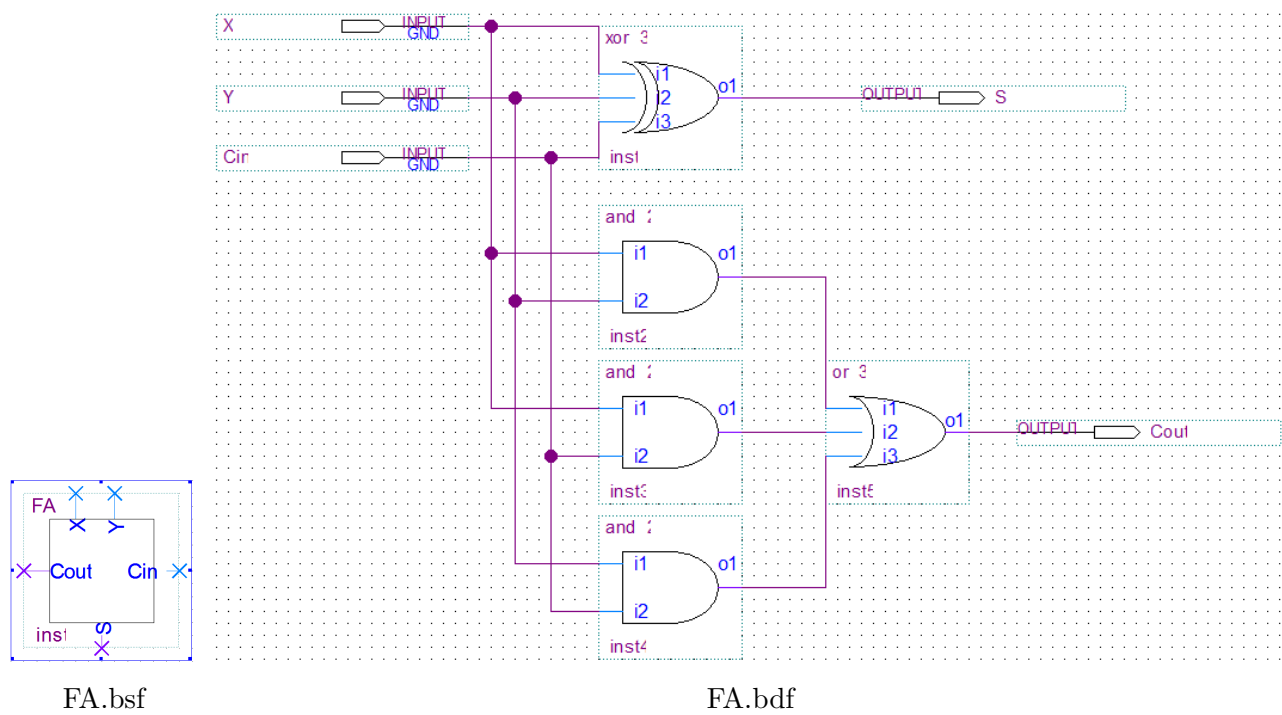


2.2 FA4: 4-bit Adder

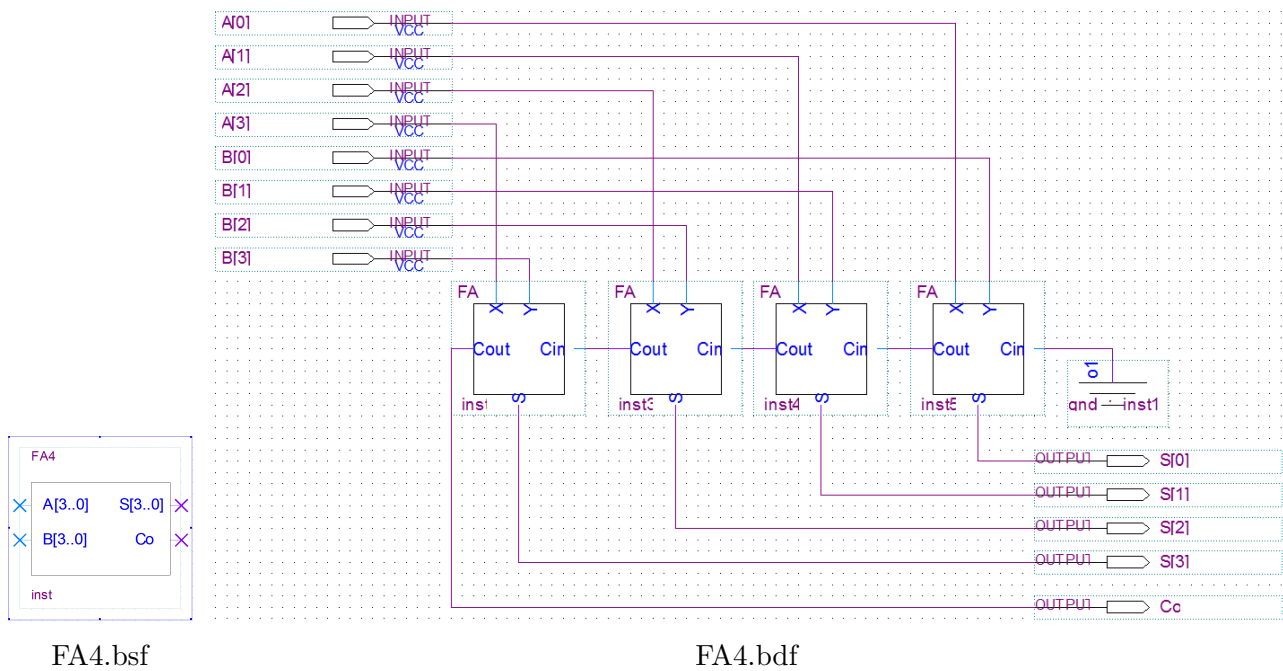


2.3 MUX1: 1-bit 2-to-1 Multiplexer

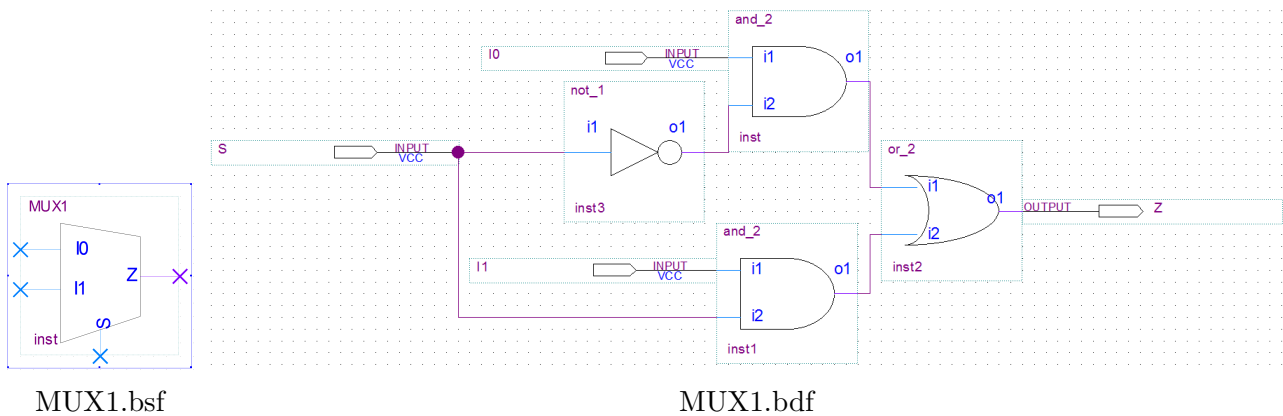


2.4 MUX4: 4-bit 2-to-1 Multiplexer

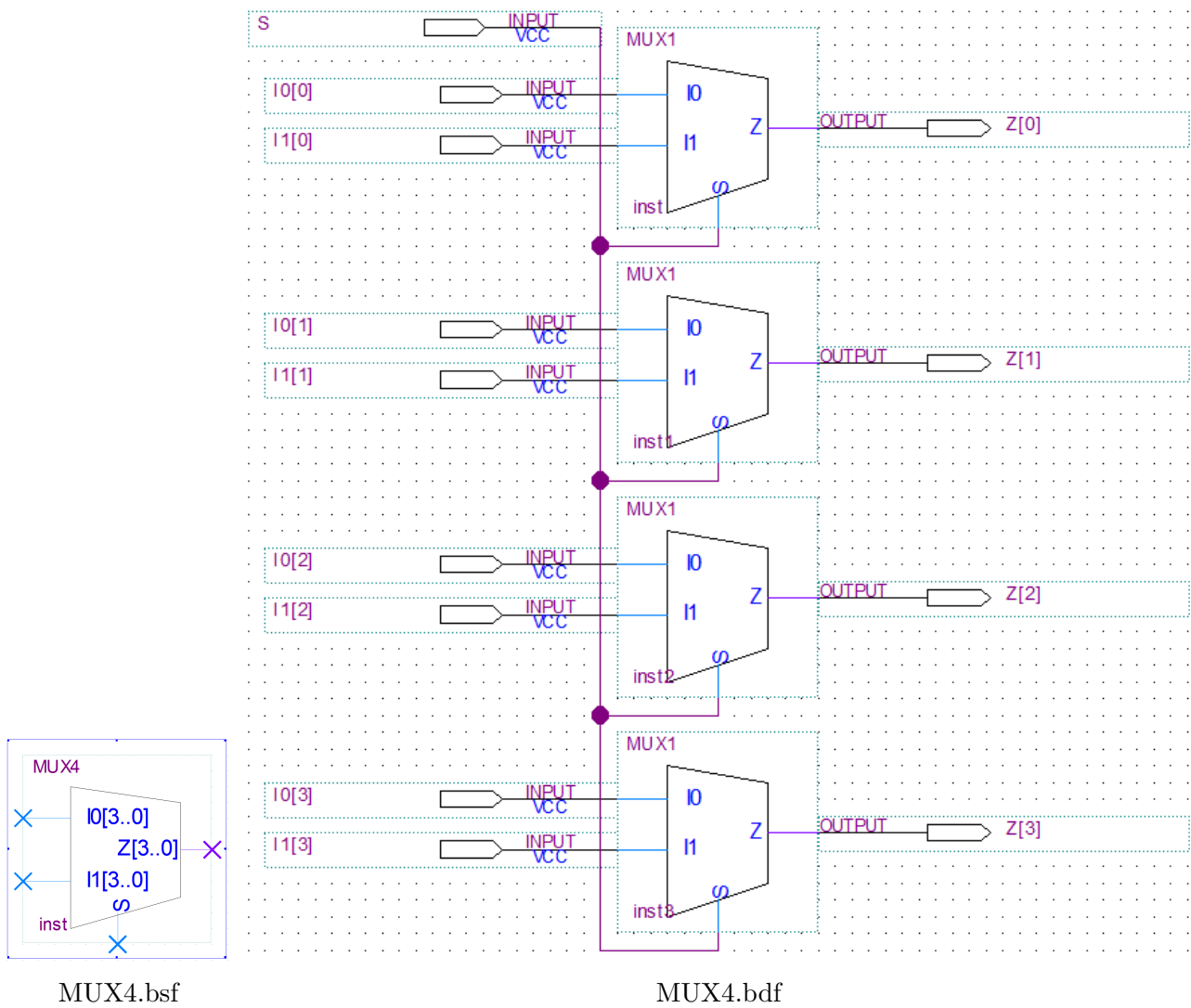


2.5 Register: 4-bit Register

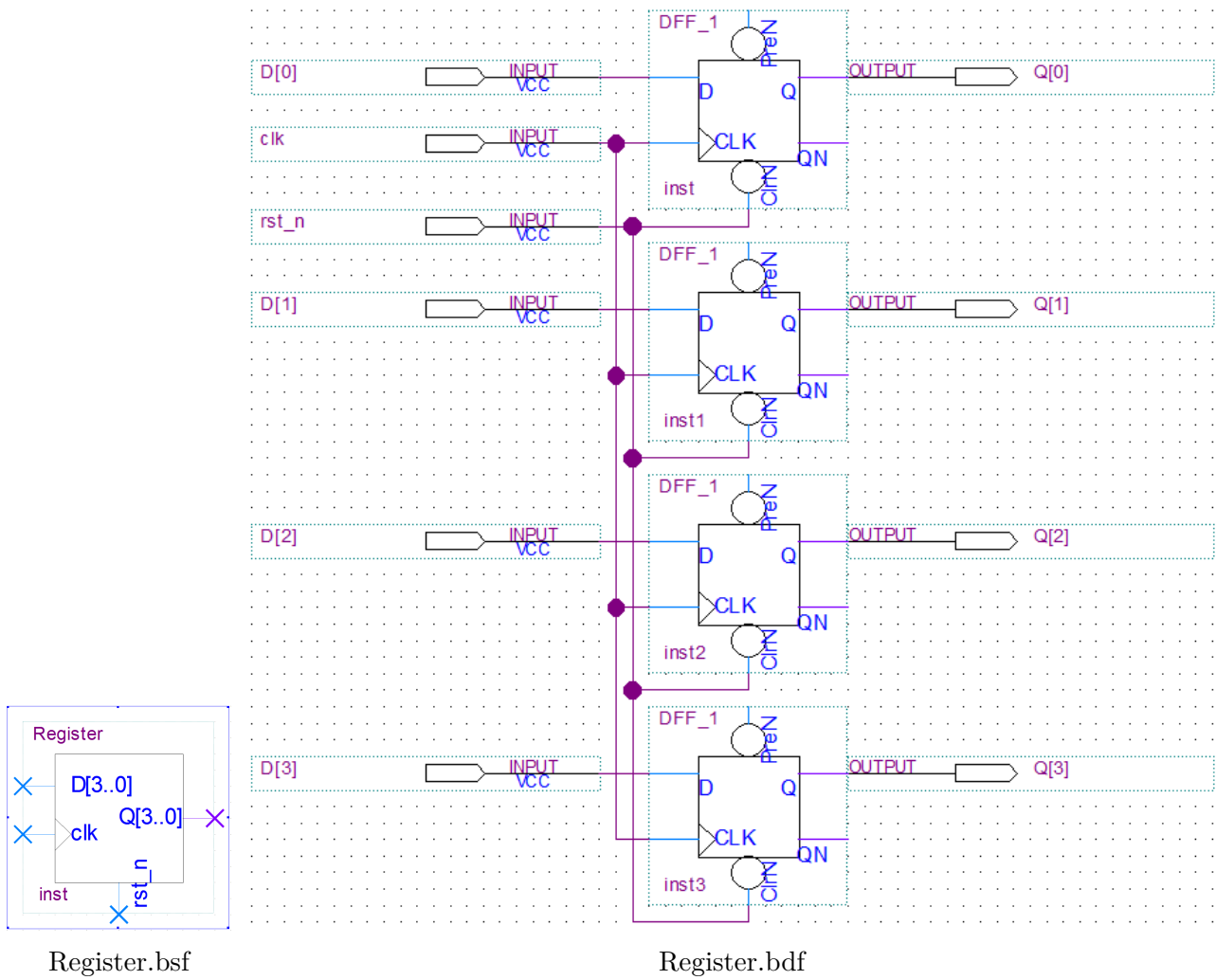

2.6 Controller: Finite-state Machine

 


Controller.bsf

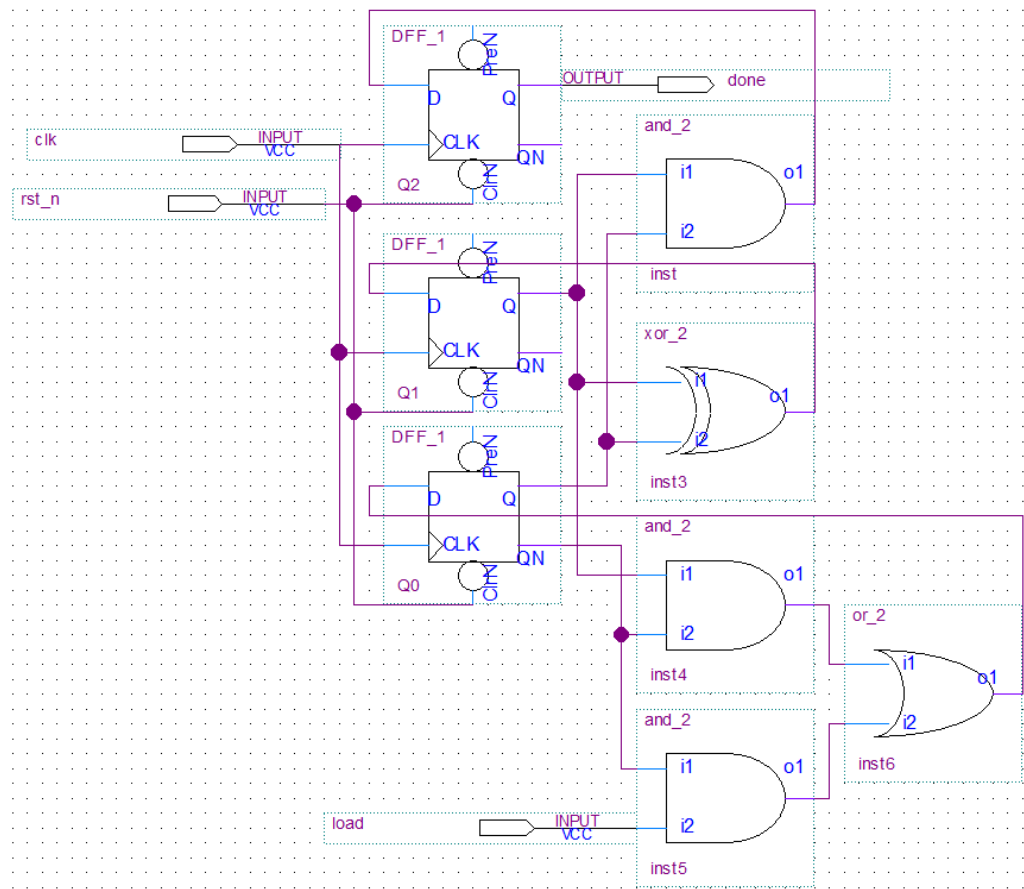


Controller.bdf

2.7 AC4: 4-bit Accumulator

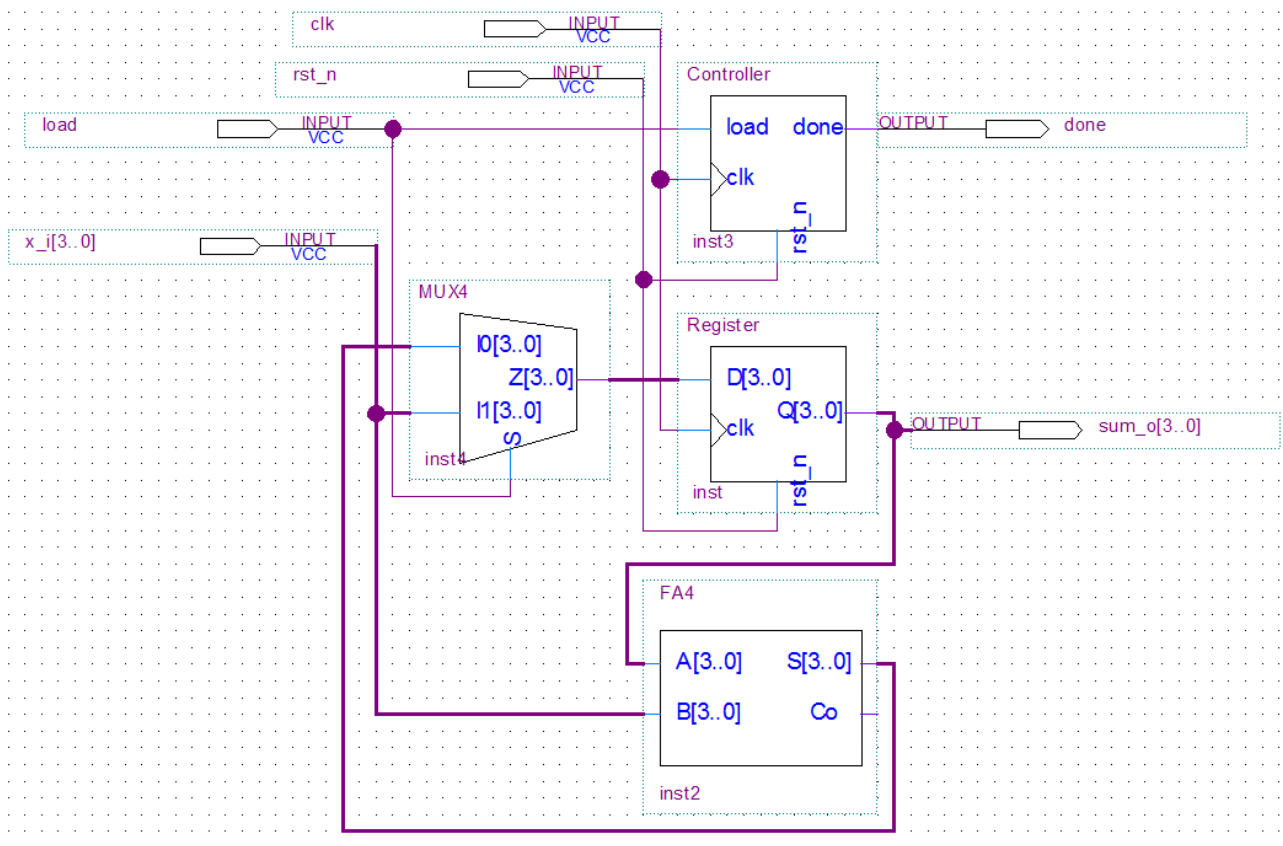


AC4.bdf

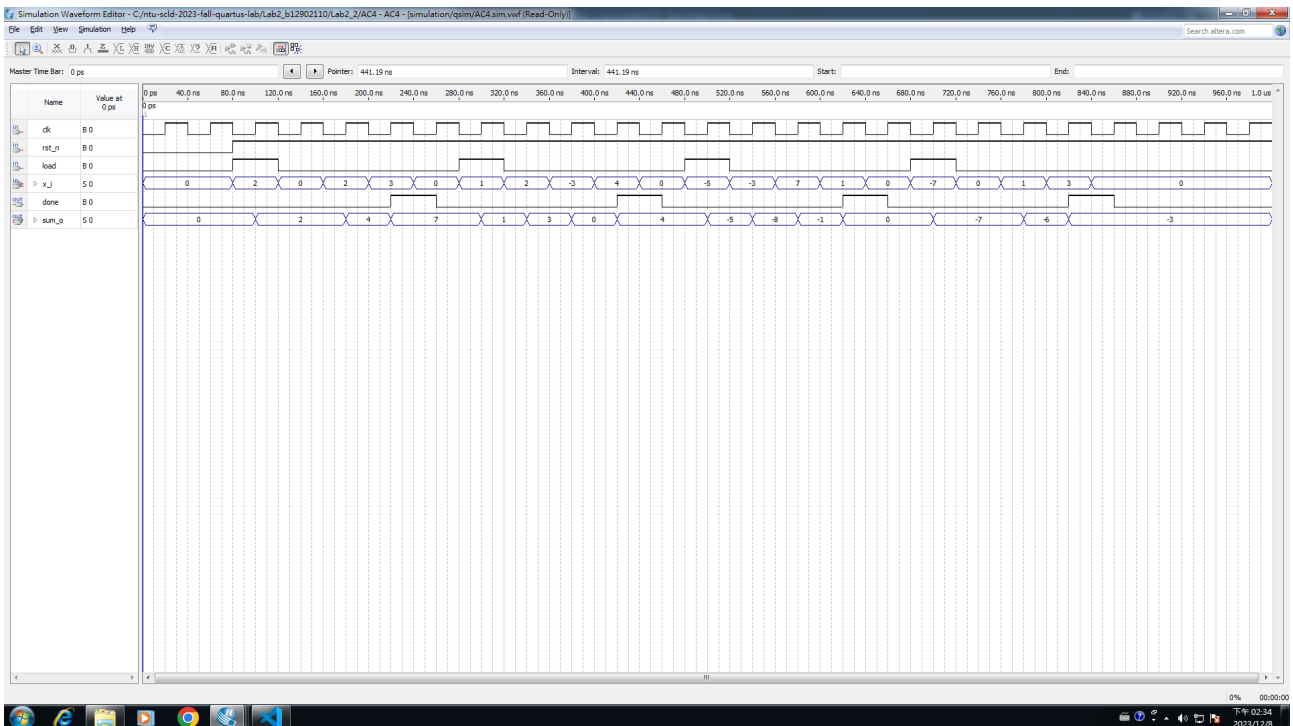


AC4 simulation result

3 Lab2_3


3.1 FA: 1-bit Full Adder

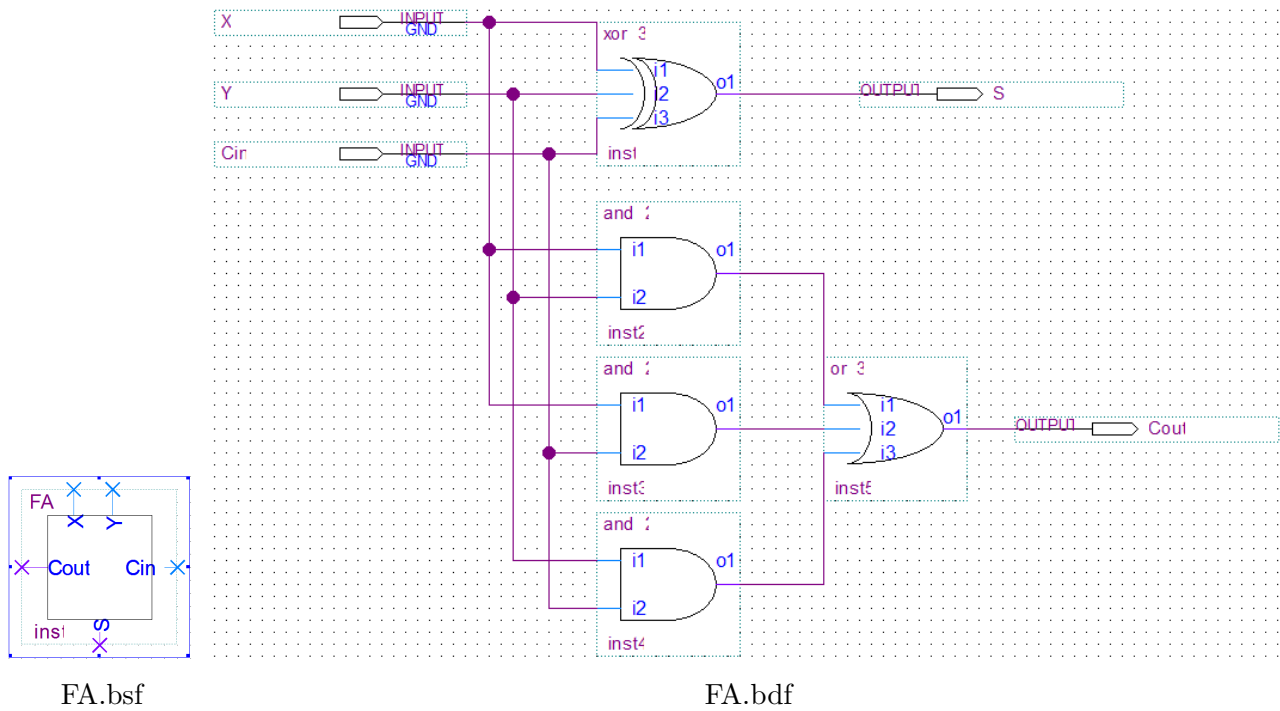


3.2 FA4: 4-bit Adder

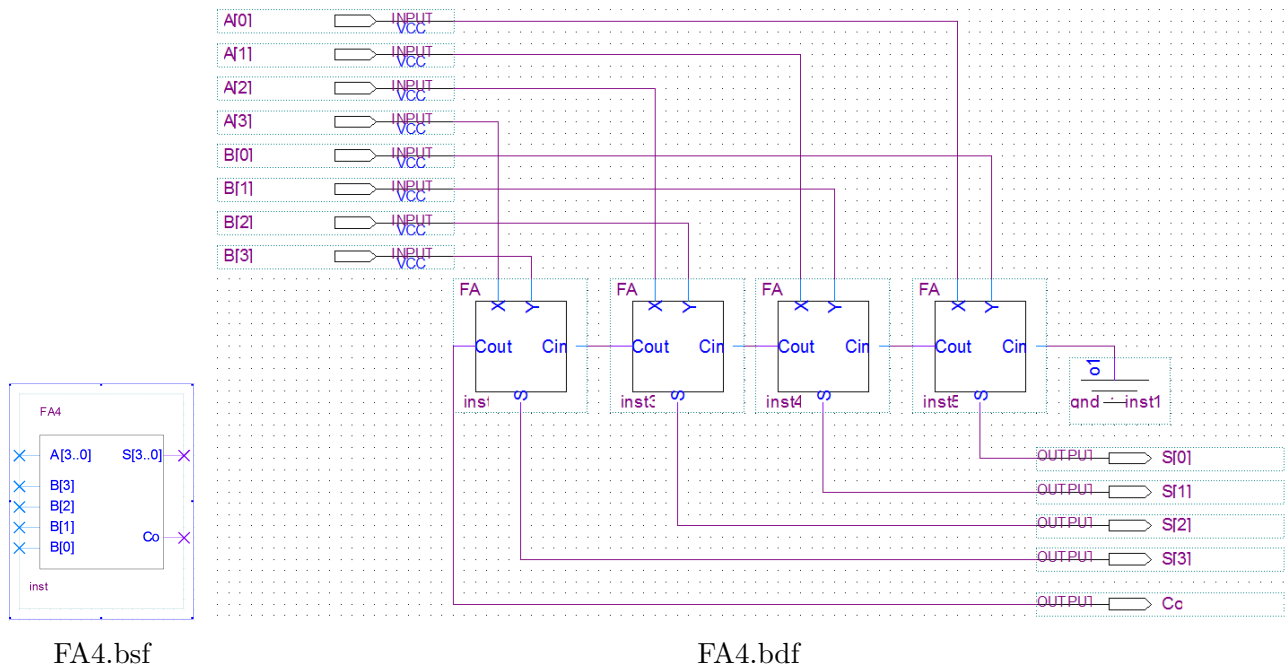


3.3 Register: 4-bit Register

 


3.4 Controller: Finite-state Machine

 

3.5 WSC: Weighted Sequence Counter

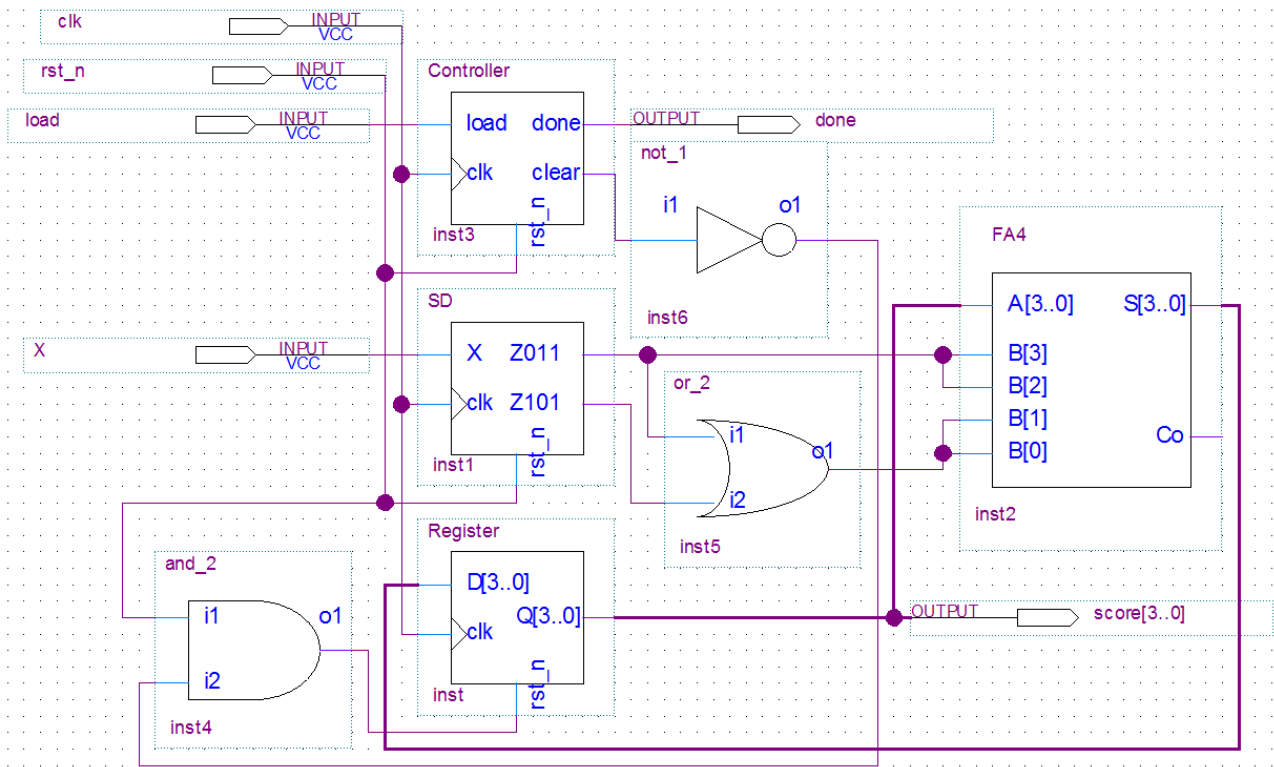

WSC.bdf

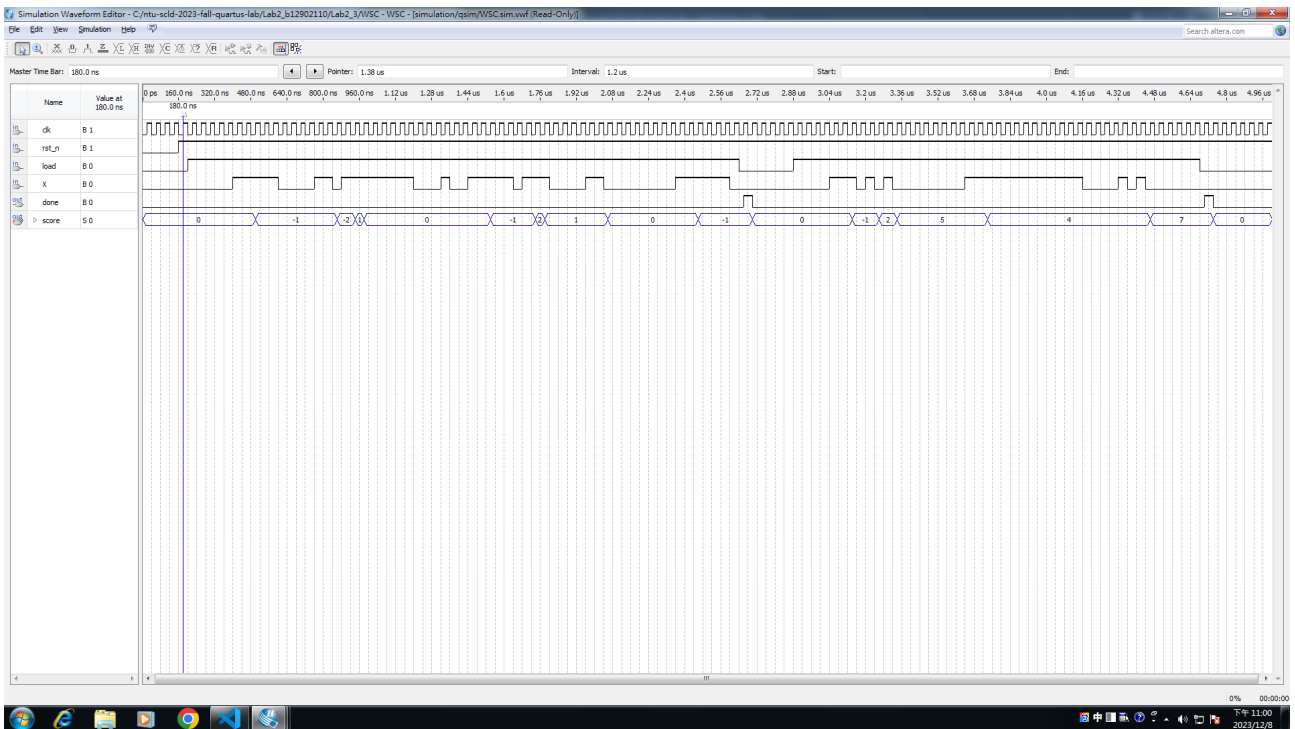

WSC simulation result